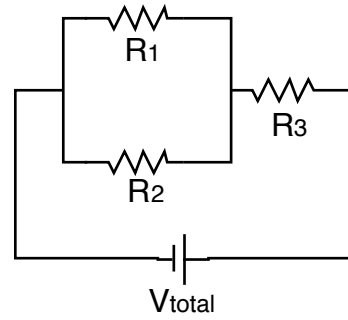


## Compound Circuits

Fill in the missing information for each of the given circuits


**Circuit 1**

|       | $R$         | $I$           | $V$ |         |
|-------|-------------|---------------|-----|---------|
| $R_1$ | $2\ \Omega$ | $1\ \text{A}$ |     | $V_t =$ |
| $R_2$ |             |               |     | $I_t =$ |
| $R_3$ | $2\ \Omega$ | $3\ \text{A}$ |     | $R_t =$ |




**Circuit 2**

|       | $R$         | $I$ | $V$           |                      |
|-------|-------------|-----|---------------|----------------------|
| $R_1$ | $4\ \Omega$ |     |               | $V_t = 12\ \text{V}$ |
| $R_2$ |             |     | $4\ \text{V}$ | $I_t =$              |
| $R_3$ | $4\ \Omega$ |     |               | $R_t =$              |

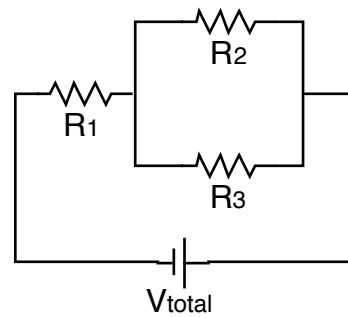


**Circuit 3**

|       | $R$         | $I$ | $V$ |                      |
|-------|-------------|-----|-----|----------------------|
| $R_1$ | $3\ \Omega$ |     |     | $V_t = 12\ \text{V}$ |
| $R_2$ | $6\ \Omega$ |     |     | $I_t =$              |
| $R_3$ | $6\ \Omega$ |     |     | $R_t =$              |

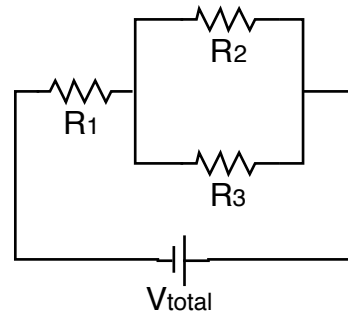

**Circuit 4**


|       | $R$         | $I$ | $V$           |                     |
|-------|-------------|-----|---------------|---------------------|
| $R_1$ | $4\ \Omega$ |     |               | $V_t =$             |
| $R_2$ |             |     | $8\ \text{V}$ | $I_t = 3\ \text{A}$ |
| $R_3$ |             |     | $4\ \text{V}$ | $R_t =$             |

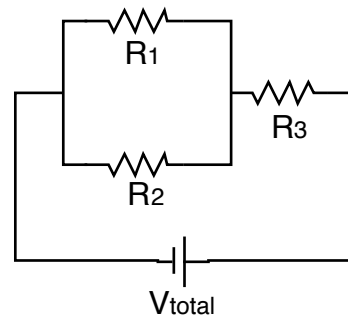

## Compound Circuits


**Circuit 5**

|                | <i>R</i> | <i>I</i> | <i>V</i> |                      |
|----------------|----------|----------|----------|----------------------|
| R <sub>1</sub> | 1 Ω      |          |          | V <sub>t</sub> = 6 V |
| R <sub>2</sub> |          |          |          | I <sub>t</sub> = 3 A |
| R <sub>3</sub> | 6 Ω      |          |          | R <sub>t</sub> =     |

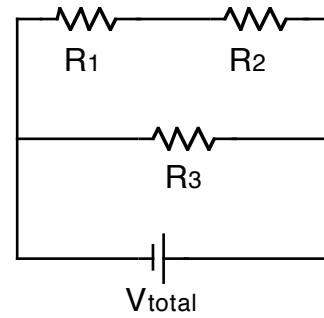


**Circuit 6**

|                | <i>R</i> | <i>I</i> | <i>V</i> |                  |
|----------------|----------|----------|----------|------------------|
| R <sub>1</sub> | 2 Ω      | 2 A      |          | V <sub>t</sub> = |
| R <sub>2</sub> | 4 Ω      |          |          | I <sub>t</sub> = |
| R <sub>3</sub> |          | 4 A      |          | R <sub>t</sub> = |

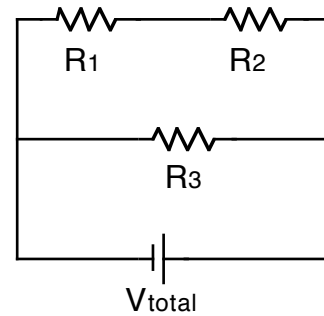

**Circuit 7**

|                | <i>R</i> | <i>I</i> | <i>V</i> |                        |
|----------------|----------|----------|----------|------------------------|
| R <sub>1</sub> | 6 Ω      |          |          | V <sub>t</sub> = 6 V   |
| R <sub>2</sub> |          | 1/6 A    |          | I <sub>t</sub> = 2/3 A |
| R <sub>3</sub> |          |          |          | R <sub>t</sub> =       |

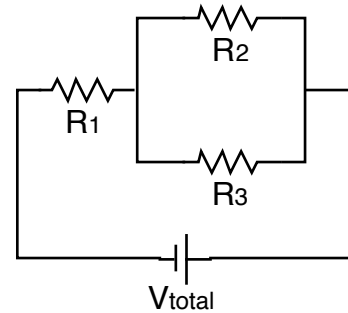

**Circuit 8**

|                | <i>R</i> | <i>I</i> | <i>V</i> |                        |
|----------------|----------|----------|----------|------------------------|
| R <sub>1</sub> |          |          |          | V <sub>t</sub> = 3 V   |
| R <sub>2</sub> |          | 1/12 A   |          | I <sub>t</sub> = 1/3 A |
| R <sub>3</sub> | 6 Ω      |          |          | R <sub>t</sub> =       |

