

Lab 35-3: Compound Circuits


- Purpose:**
1. To calculate the voltages and currents for individual resistors in a compound circuit.
 2. To calculate the actual equivalent resistance of a compound circuit.
 3. To calculate the ideal equivalent resistance of a compound circuit.
 4. To determine what happens to voltage, current and resistance in a compound circuit.
 5. To apply the ideas of conservation of charge and conservation of energy to a compound circuit.

Procedure:

1. Hook up the circuit shown in the diagram below.
2. Set the power supply for about 1 volt.
3. Measure the current and voltage for each resistor in the circuit and record in the data table.
4. Measure the total voltage and total current using your portable meters.

Remember: Ammeters are connected in series. Voltmeters are connected in parallel.

Circuit 1 Diagram:

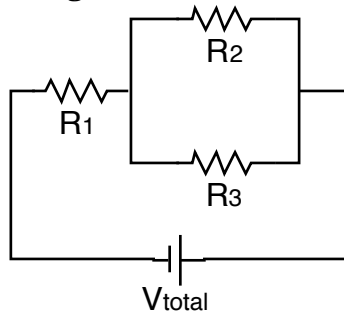


Data:

	R	V	I
R ₁	2 Ω		
R ₂	5 Ω		
R ₃	2 Ω		

V _{power supply}	
I _{power supply}	

Questions:

1. The current in R₁ should have been the same as the current leaving the power supply. Why?
2. The current going through R₁ should have been equal to the sum of the current in R₂ and R₃. Why?
3. The voltages of two resistors should be the same. Which two are they and why should they be the same?

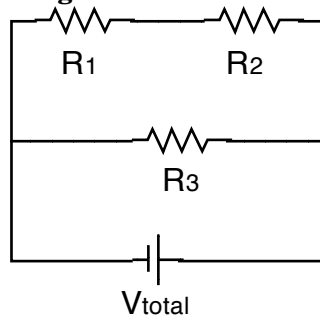Lab 35-3: Compound Circuits**Circuit 2 Diagram:****Data:**

	R	V	I
R_1	2 Ω		
R_2	5 Ω		
R_3	2 Ω		

$V_{power\ supply}$	
$I_{power\ supply}$	

Questions:

- The voltage of R_3 should be the same as the voltage of the power supply. Why?
- The currents through R_1 and R_2 should be the same. Why is that?
- How does the current leaving the power supply compare to the currents through the top branch and the bottom branch of the circuit?