

Resistance and Ohm's Law

1. The resistance of your body can vary a great amount, depending on how dry or sweaty you are.
 - a. If the resistance of your body was $100,000 \Omega$, how much current would flow through your body if you touched the ends of a 24 volt potential?

 - b. What would be your resistance if your body drew 0.1 amp of current from a 48 V potential? (This current through your heart would probably kill you.)

2. A 75 W light bulb is in a 120 V outlet.
 - a. What is the current drawn by the light bulb?

 - b. What is the resistance of the light bulb?

 - c. How many electrons would pass through the light bulb in one hour?

3. There is a current of 3 amps passing through a 25Ω resistor.
 - a. What is the potential difference across the resistor?

 - b. What power is dissipated by the resistor?

 - c. How much energy is dissipated by the resistor in 30 minutes?

4. A hair dryer is plugged into a 120 V outlet and draws 4 amps of current.
 - a. What is the power of the hair dryer?

 - b. What is the resistance of the hair dryer?

- *5. A flashlight has a 10 W bulb in it with a resistance of 2.03Ω when it is lit.
 - a. What current would the bulb draw?

 - b. How many 1.5 V batteries would be needed for this flashlight?

Answers: 1.a) 0.00024 A b) 480Ω 2.a) 0.63 A b) 192Ω c) 1.42×10^{22} 3.a) 75 V b) 225 W
 c) $405,000 \text{ J}$ 4.a) 480 W b) 30Ω 5.a) 2.22 A b) $4.5 \text{ V}; 3 \text{ batteries}$