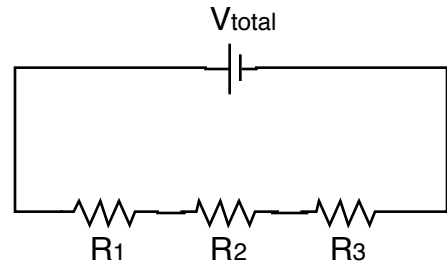


Circuit Worksheet Answers

For each of the given circuits, calculate the equivalent resistance. Then, calculate the total current. Finally, calculate the individual currents and voltages for each resistor.

Circuit 1




	<i>R</i>	<i>I</i>	<i>V</i>	
R ₁	3 Ω	1	3	V _{total} = 9 v
R ₂	3 Ω	1	3	I _{total} = 1
R ₃	3 Ω	1	3	R _{total} = 9

Circuit 2



	<i>R</i>	<i>I</i>	<i>V</i>	
R ₁	12 Ω	1/2	6	V _{total} = 6 v
R ₂	12 Ω	1/2	6	I _{total} = 3/2
R ₃	12 Ω	1/2	6	R _{total} = 4

Circuit 3

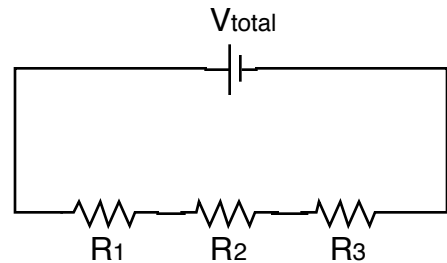

	<i>R</i>	<i>I</i>	<i>V</i>	
R ₁	4 Ω	1/2	2	V _{total} = 9 v
R ₂	8 Ω	1/2	4	I _{total} = 1/2
R ₃	6 Ω	1/2	3	R _{total} = 18


Circuit Worksheet Answers

Circuit 4




	<i>R</i>	<i>I</i>	<i>V</i>	
R ₁	6 Ω	1	6	V _{total} = 6 v
R ₂	12 Ω	1/2	6	I _{total} = 7/2
R ₃	3 Ω	2	6	R _{total} = 12/7

Circuit 5

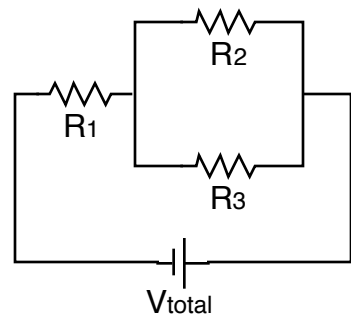

	<i>R</i>	<i>I</i>	<i>V</i>	
R ₁	4 Ω	2	8	V _{total} = 12 v
R ₂	4 Ω	1	4	I _{total} = 2
R ₃	4 Ω	1	4	R _{total} = 6


Circuit 6

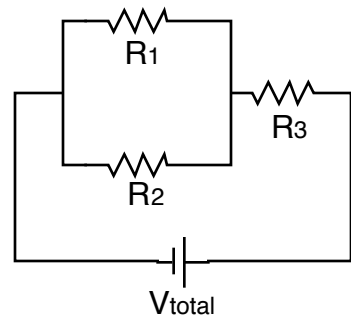

	<i>R</i>	<i>I</i>	<i>V</i>	
R ₁	6 Ω	1/3	2	V _{total} = 9 v
R ₂	3 Ω	2/3	2	I _{total} = 1
R ₃	7 Ω	1	7	R _{total} = 9


Circuit Worksheet Answers

Circuit 7

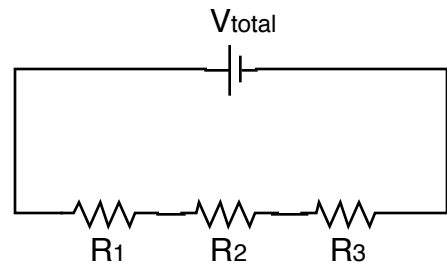


	R	I	V	
R_1	1	2	2 v	$V_{total} = 18$ $I_{total} = 2$ a $R_{total} = 9 \Omega$
R_2	5	2	10 v	
R_3	3 Ω	2	6	

Circuit 8

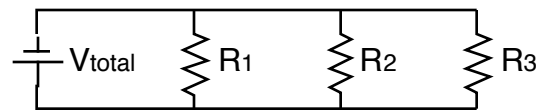

	R	I	V	
R_1	8 Ω	1/2	4	$V_{total} = 4$ $I_{total} = 4$ a $R_{total} = 1 \Omega$
R_2	2	2 a	4	
R_3	8/3	3/2	4	


Circuit 9

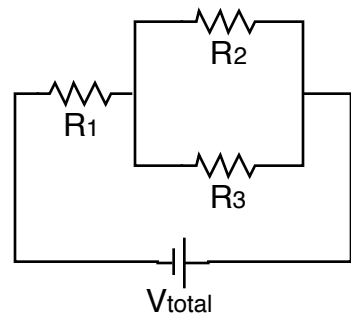

	R	I	V	
R_1	4/3	3	4 v	$V_{total} = 12$ $I_{total} = 3$ a $R_{total} = 4$
R_2	4 Ω	2	8	
R_3	8	1	8 v	

Circuit Worksheet Answers

Circuit 10

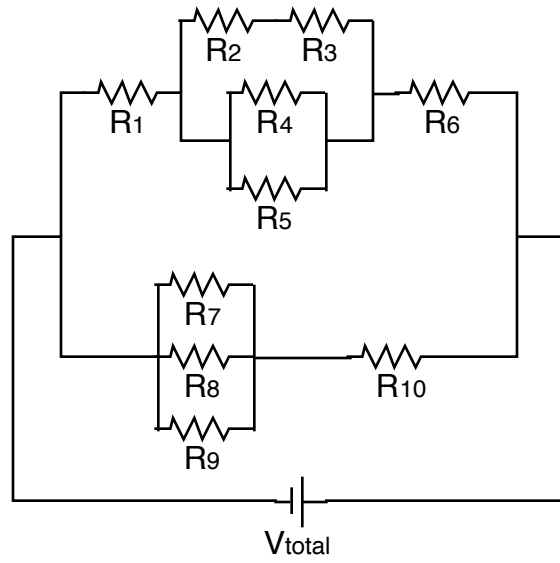

	R	I	V	
R_1	1Ω	$7/2$	$7/2$	$V_{total} = 18 \text{ v}$
R_2	3Ω	$1/2$	$3/2$	$I_{total} = 11/2$
R_3	5Ω	$1/2$	$5/2$	$R_{total} = 36/11$
R_4	2Ω	2	4	
R_5	4Ω	1	4	
R_6	3Ω	$7/2$	$21/2$	
R_7	5Ω	$4/5$	4	
R_8	5Ω	$4/5$	4	
R_9	10Ω	$2/5$	4	
R_{10}	7Ω	2	14	