

## Resistance and Ohm's Law

---

1. The resistance of your body can vary a great amount, depending on how dry or sweaty you are.
  - a. If the resistance of your body was  $100,000 \Omega$ , how much current would flow through your body if you touched the ends of a 24 volt potential?
  
  - b. What would be your resistance if your body drew 0.1 amp of current from a 48 V potential? (This current through your heart would probably kill you.)
  
2. A 75 W light bulb is in a 120 V outlet.
  - a. What is the current drawn by the light bulb?
  
  - b. What is the resistance of the light bulb?
  
  - c. How many electrons would pass through the light bulb in one hour?
  
3. There is a current of 3 amps passing through a  $25 \Omega$  resistor.
  - a. What is the potential difference across the resistor?
  
  - b. What power is dissipated by the resistor?
  
  - c. How much energy is dissipated by the resistor in 30 minutes?
  
4. A hair dryer is plugged into a 120 V outlet and draws 4 amps of current.
  - a. What is the power of the hair dryer?
  
  - b. What is the resistance of the hair dryer?
  
5. A flashlight has a 10 W bulb in it with a resistance of  $2.03 \Omega$  when it is lit.
  - a. What current would the bulb draw?
  
  - b. How many 1.5 V batteries would be needed for this flashlight?

Answers:    1.a)  $0.00024 \text{ A}$     b)  $480 \Omega$     2.a)  $0.63 \text{ A}$     b)  $192 \Omega$     c)  $1.42 \times 10^{22}$     3.a)  $75 \text{ V}$  b)  $225 \text{ W}$   
               c)  $405,000 \text{ J}$     4.a)  $480 \text{ W}$     b)  $30 \Omega$     5.a)  $2.22 \text{ A}$     b)  $4.5 \text{ V}; 3 \text{ batteries}$